



# ENGG1000


Electrical Stream 2018

Lecture Week 4 – Power Sources and Regulators

Never Stand Still

Faculty of Engineering

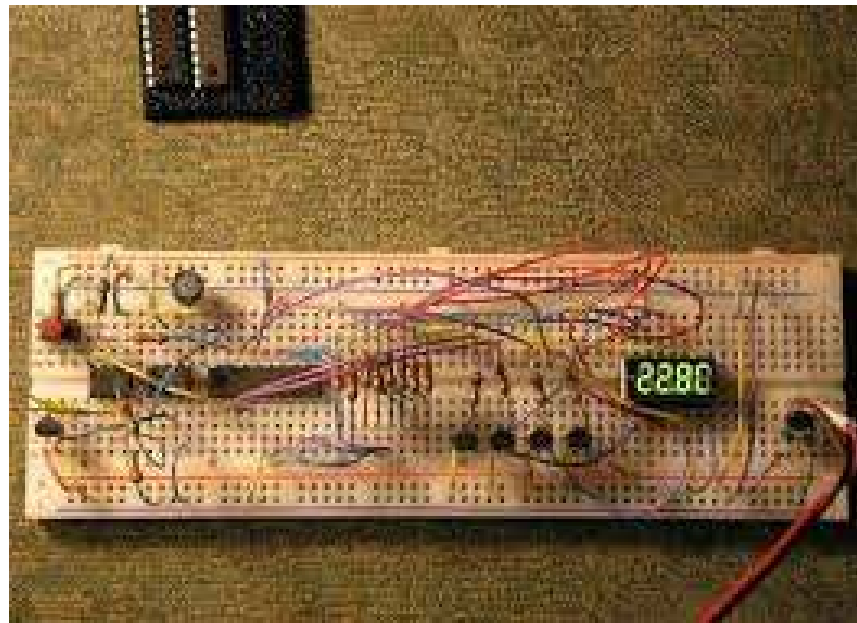School of Electrical Engineering and Telecommunications




# Advice from Students from Previous Years

- Start early and test as much as possible. When you find a flaw, fix it to the maximum extent possible. None of this "It probably won't be a problem.." stuff.
- The internet is a great source of info
- Learnt that organisation is very necessary in all activities
- It is always better to begin early rather than regret later
- Learnt to rely on and trust my team members
- Do not expect your design to work every time
- Use components that will actually work properly with each other
- Building this was fun :P
- Working as a team is vital
- COMMUNICATION.....something there wasn't enough of
- an initial plan would have been helpful
- Testing is paramount to success.....test that \*\*\*\*\* as many times as you can!
- construction should start asap to allow sufficient testing
- be prepared to modify ur design during the construction stage, you are bound to run into small complications that you didn't foresee
- everyone needs to get involved, many hands make light work
- keep everything as simple as possible
- if things can go wrong, they usually happen at the worst time

# Fundamental Laws - KVL


- Conservation of energy
- The sum of voltages around any closed loop in a circuit must be zero

$$V_1 + V_2 + V_3 + \dots = 0$$

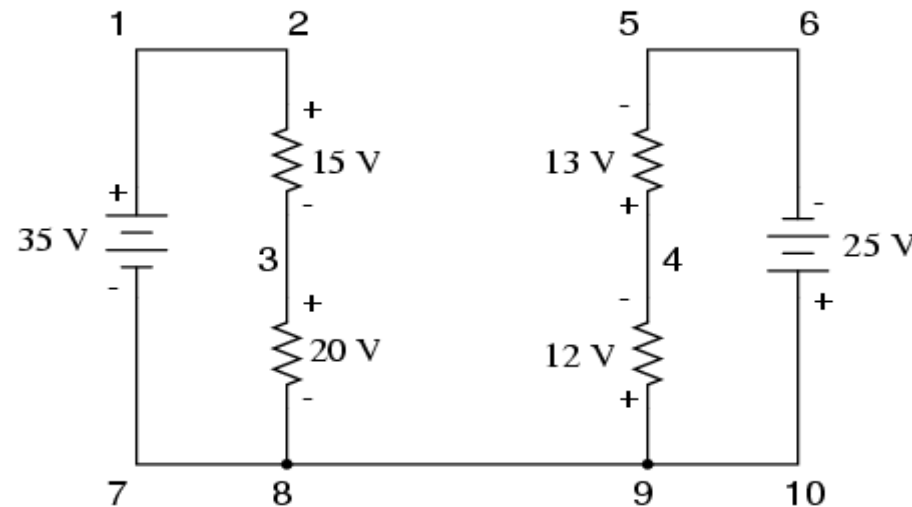
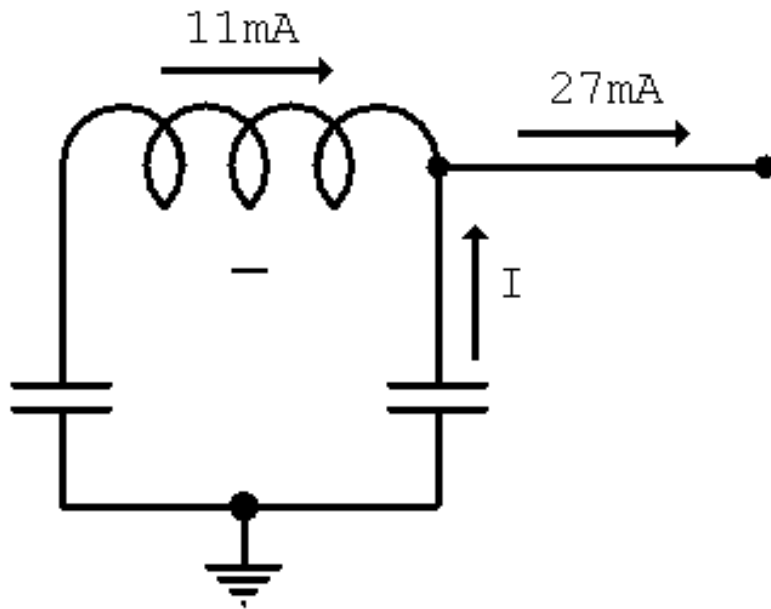
# Fundamental Laws - KCL

- Conservation of Electrical charge
- The net current flowing into any junction is always equal to the net current flowing out




$$I_1 + I_2 + I_3 + \dots = 0$$

# Voltage, Current and Resistance

- The simplest is for current and voltage to be linearly related
- Ohm's Law

$$V = IR$$

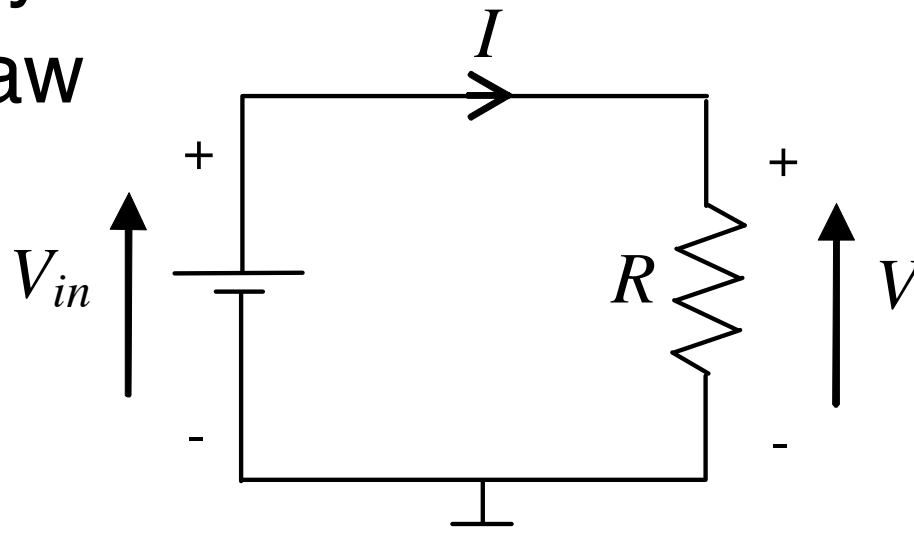


- Current  $I$  is the flow of positive charge through the circuit in Amps (A)

# Resistive Circuits

- Resistors connected in series **increase** the total equivalent resistance


$$R = R_1 + R_2 + \dots + R_N$$

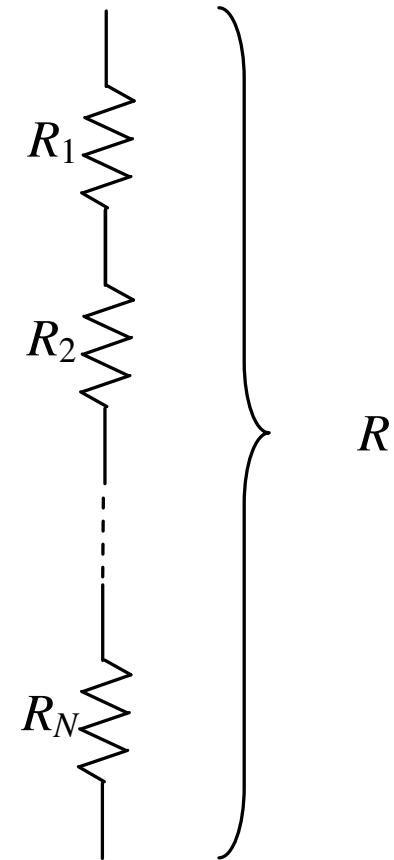

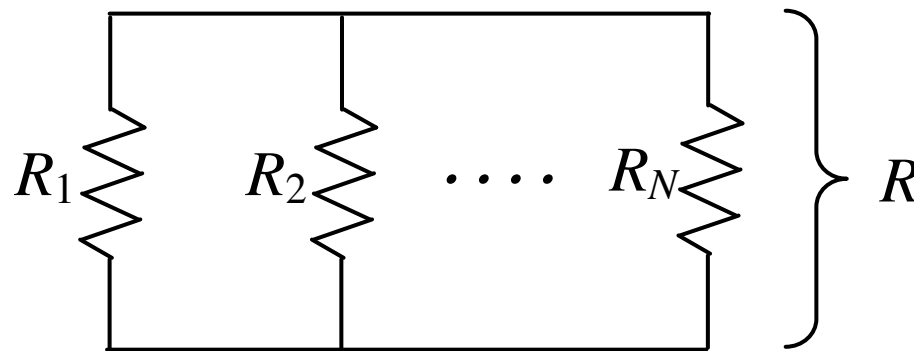
# Resistive Circuits

- Resistors connected in parallel **decrease** the total equivalent resistance

$$R = R_1 // R_2 // \dots // R_N = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$



# A Problem

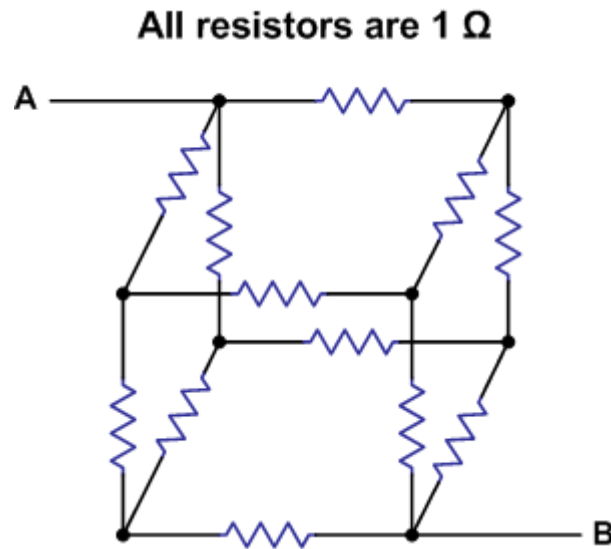

What is the resistance between A and B?




# The Voltage Divider

- Assume there is no  $R_L$  ( $R_L = \infty$ )

$$V = IR_2 \quad \text{and} \quad I = \frac{V_{in}}{R_1 + R_2}$$


so

$$V = \frac{R_2}{R_1 + R_2} V_{in}$$

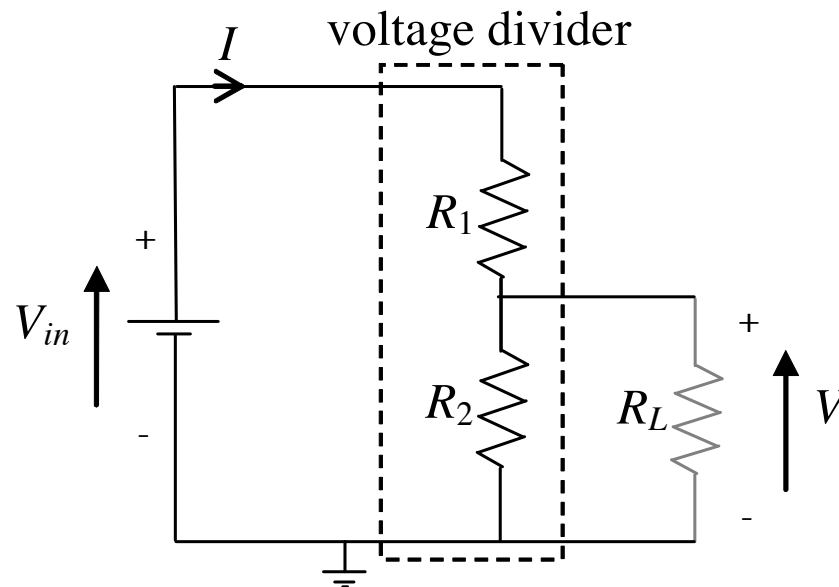
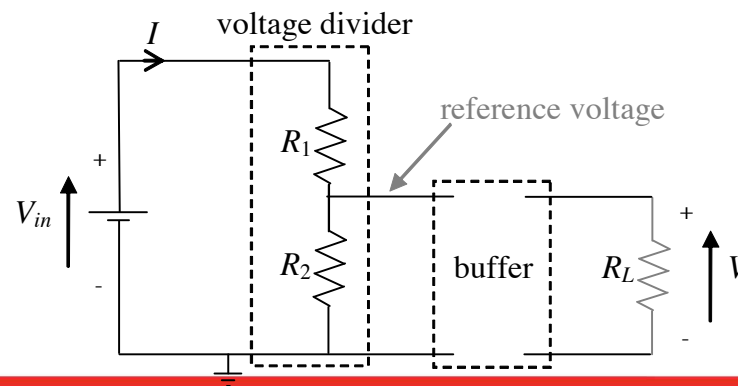
# The Voltage Divider


- Can use this circuit to step down voltages by a constant factor  $\frac{R_2}{R_1 + R_2}$
- Take care: in practice  $R_L \neq \infty$   $V = \frac{R_2 // R_L}{R_1 + R_2 // R_L} V_{in}$ 
  - Small  $R_L \Rightarrow$  affects the voltage division
  - Large  $R_L \Rightarrow$  most power dissipated in divider
- Voltage divider good as reference voltage



# Voltage Sources

- Real voltage sources have internal resistance
- When a load is connected, the supplied voltage is really

$$V_O = \frac{R_L}{R_S + R_L} V_S$$

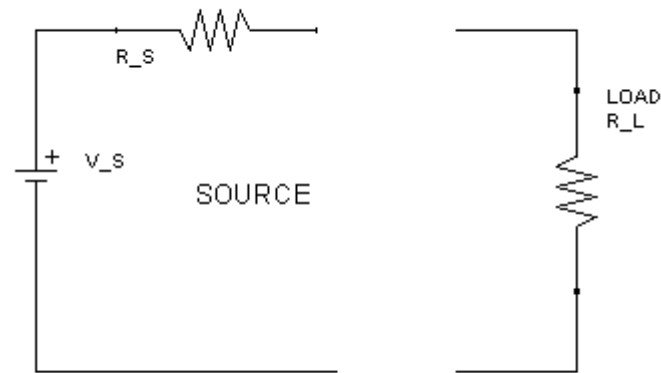


- The ideal is  $R_L \gg R_S$
- Important to realise this when you drive one circuit by another – may not always be possible!

# Voltage Sources


- Practical Solutions for Buffers:
  - Zener Diodes
  - Transistors
  - Operational Amplifiers
- Aim of a 'Buffer':
  - From the view of the Load, make the source impedance  $\rightarrow 0$
  - Source provides same voltage, regardless of how much current is drawn
  - From the view of the Source, make the load impedance very large
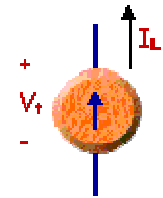
# Current Sources

- By analogy, can also construct current sources
  - Will use transistors and op-amps (later)
- An ideal current source can supply the same current, regardless of the load that is attached




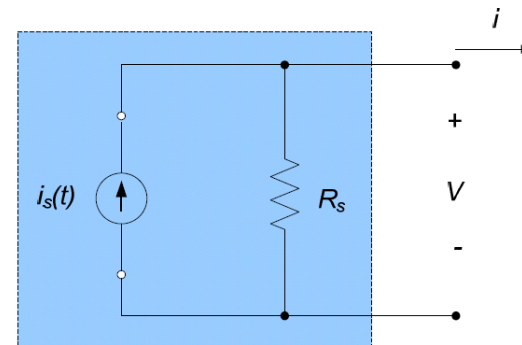
- Non-ideal current source offers some level of shunt(parallel) resistance



# Diodes


- $V_D < V_{on}$ 
  - Diode is reverse-biased
    - i.e. “off” or acts as an open circuit
- $V_D > V_{on}$ 
  - Diode is forward-biased
    - i.e. “on” or acts as a short circuit
- Summary: a diode conducts current in one direction
  - Good for protecting sensitive components
- Caveat:  $V_{on} \approx 0.6$  to  $0.7V$

# How?

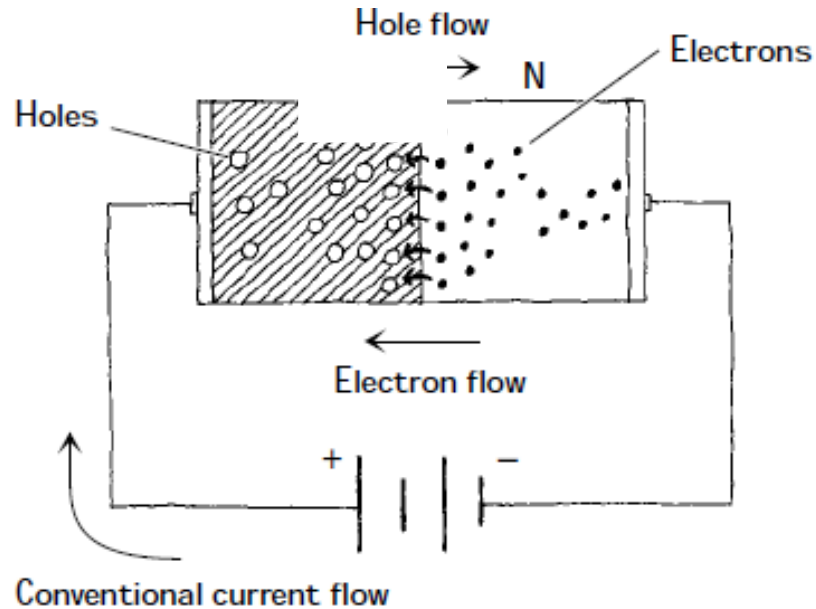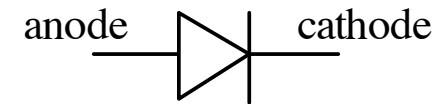

- Forward biased  
– conductor

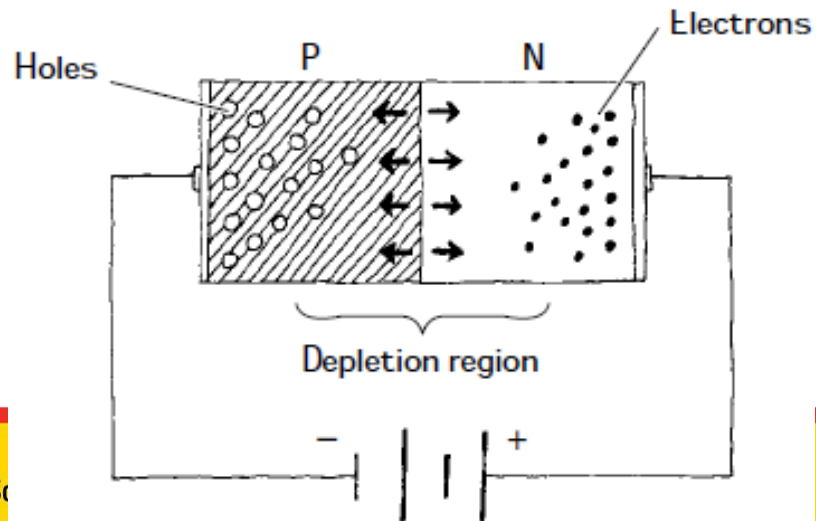N: has 'spare' electrons  
P: has 'missing' electrons




- Reverse biased  
– insulator

Diode properties can be *electrically* controlled

source: Scherz, 2000
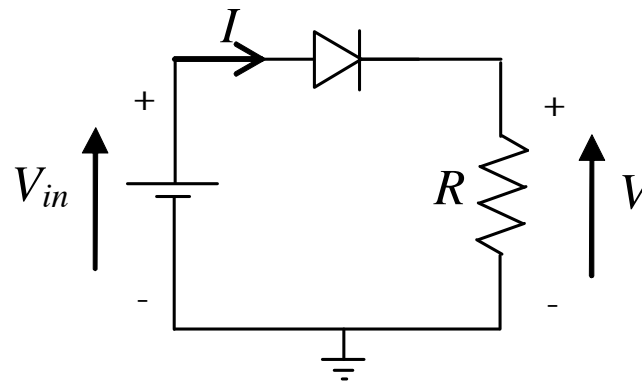
# Analysis of Diode Circuits


- Split into two cases:
- $V_{in} < V_{on}$ 
  - No current flows through diode  $\Rightarrow V = 0$
- $V_{in} > V_{on}$ 
  - Diode has voltage  $V_D = V_{on}$ , so  $V = V_{in} - V_{on}$   
and 
$$I = \frac{V}{R} = \frac{V_{in} - V_{on}}{R}$$





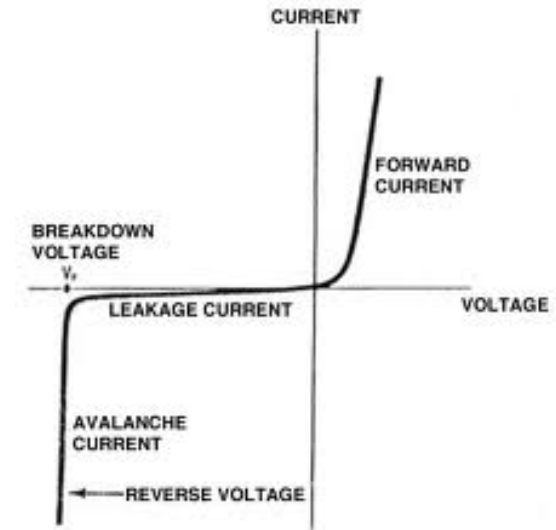
# Real Diodes

- True I-V relationship:
- The forward current does increase slightly as the voltage increases
- There is a reverse leakage current
  - Due to the thermal creation of electron-hole pairs
- As previously stated, it can break down if the reverse voltage is very large
  - A normal diode will not recover



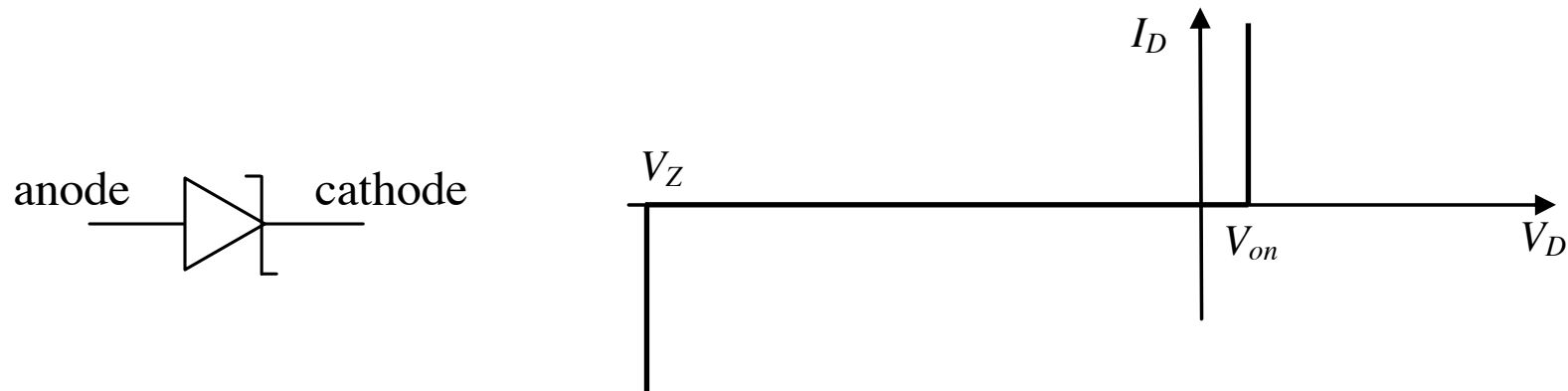
# Zener Diodes

- Zener diodes are similar to diodes, but have another property known as reverse breakdown
  - Seen from current-voltage relationship


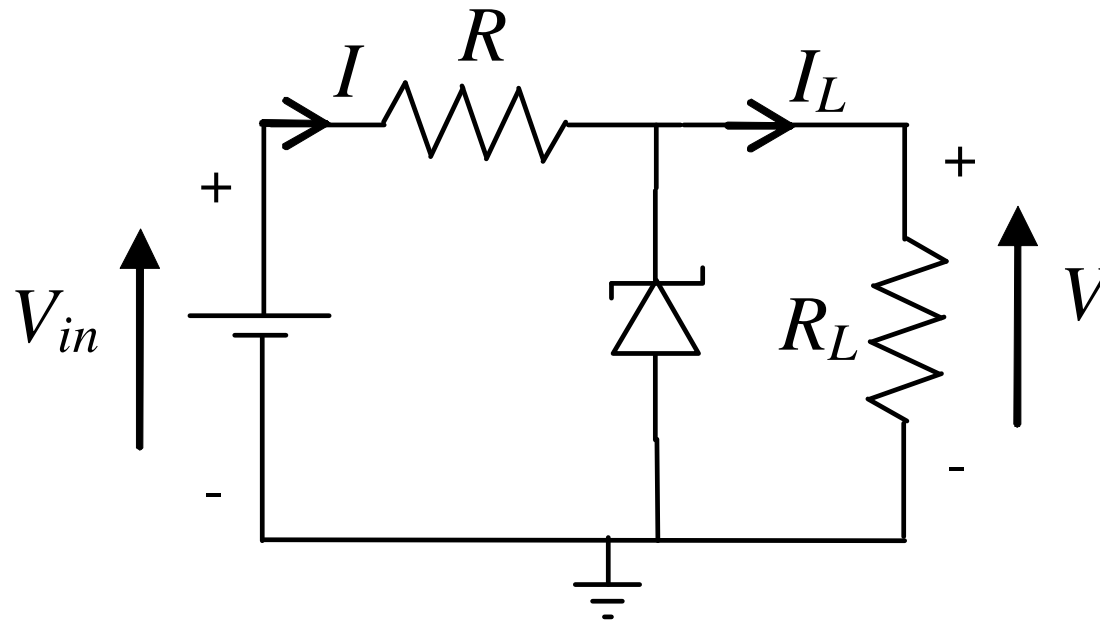
# Zener Applications



- Used in voltage regulation
  - e.g. if  $V_{in} = 6V$ ,  $V_Z = 5V$  then the circuit below steps the input voltage down to  $V = V_Z$



Better still for voltage regulation: Regulator integrated circuits like the LM7805 or the LM317

# Zener Diode Regulation

- Handles changes in load supply

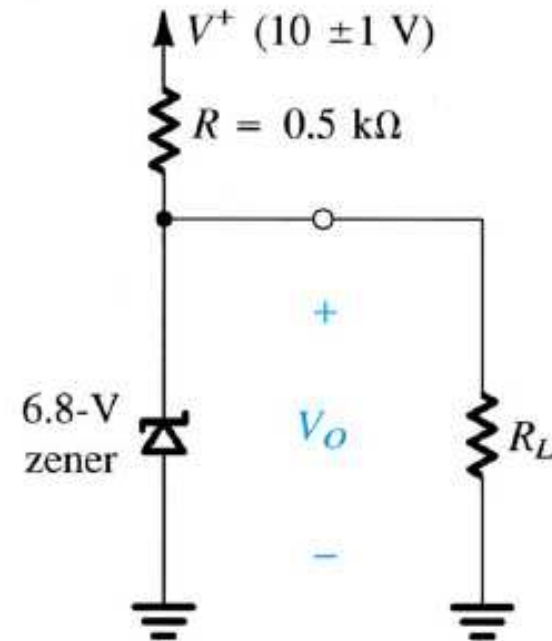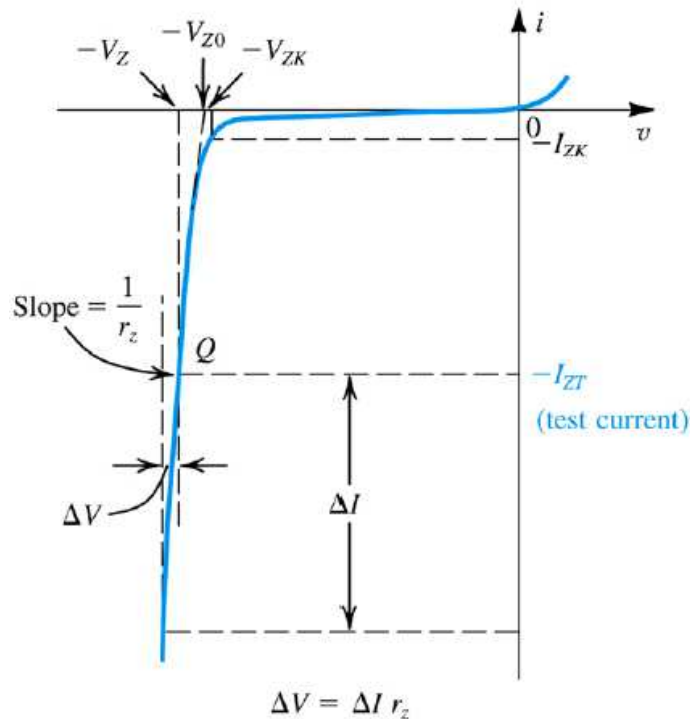

# Which power supply?

- Bench-top
  - Use if system “mains powered”
- Batteries
  - Portable system
  - Alkaline, NiMH, Li-Ion?
  - In-circuit charger?
- Linear Regulators
  - Easy to design
  - Available for fixed and variable voltages
- Switch-mode
  - Much better efficiency than linear regulators
  - Harder to design
  - Some ICs available

# Voltage Regulators

- Aim
  - Maintain a stable output voltage, given variations in output load and fluctuations in the input voltage
- Regulated Supply - Contain a reference voltage
  - Zener diode?
  - Output voltage compared to reference voltage
  - Feedback then used
- Two main types
  - Linear Voltage Regulators
  - Switch-mode Voltage Regulators


# Voltage Reference

Typically use Zener diodes

These are quite noisy

- avalanche noise
- use capacitors to remove high-frequency noise

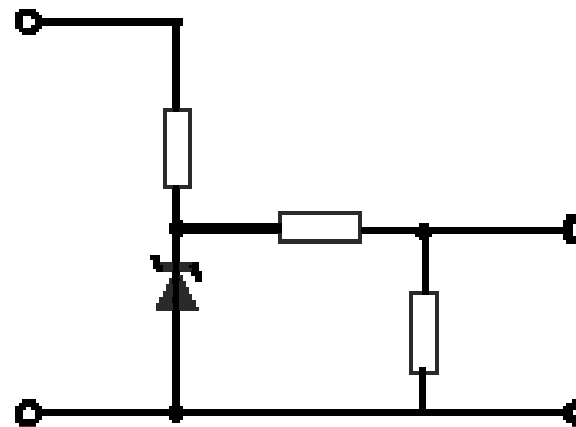- Tantalum capacitor in series with the output removes noise spikes





# Linear Voltage Regulator

## Series Topology
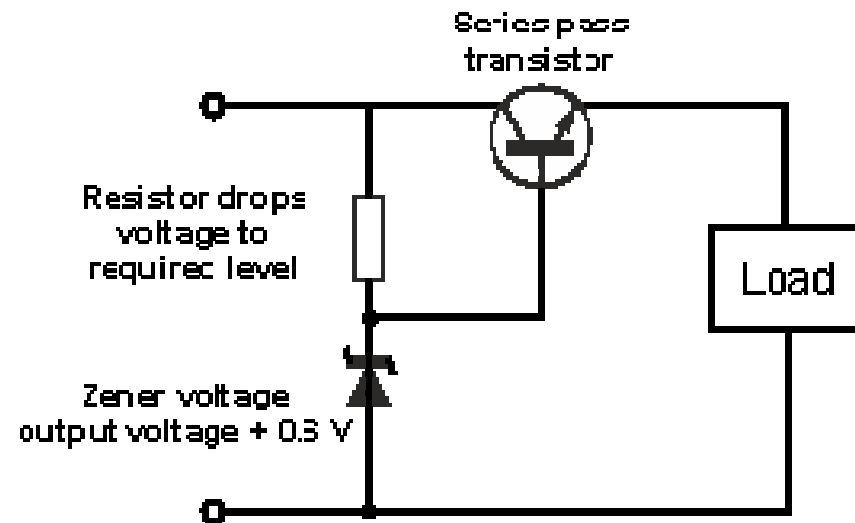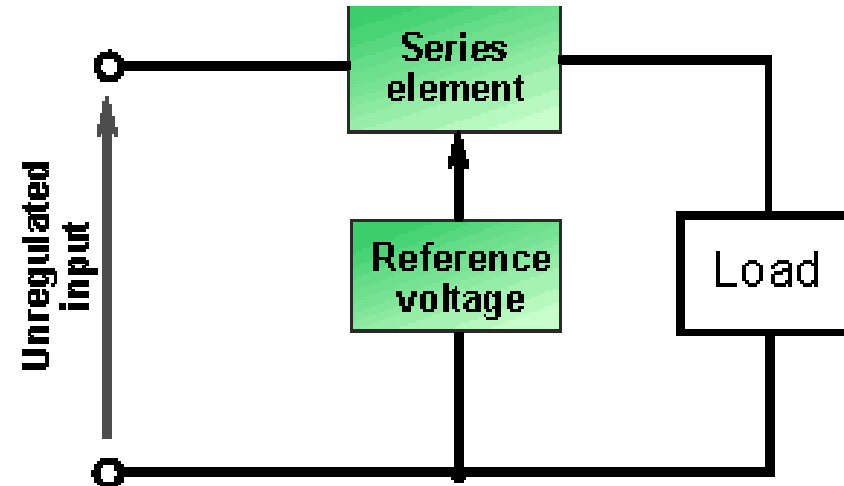
## Design Considerations

- Consider max and min load currents
- Zener will require a certain current to remain RBD
- Max power that Zener can dissipate






# Linear Voltage Regulator
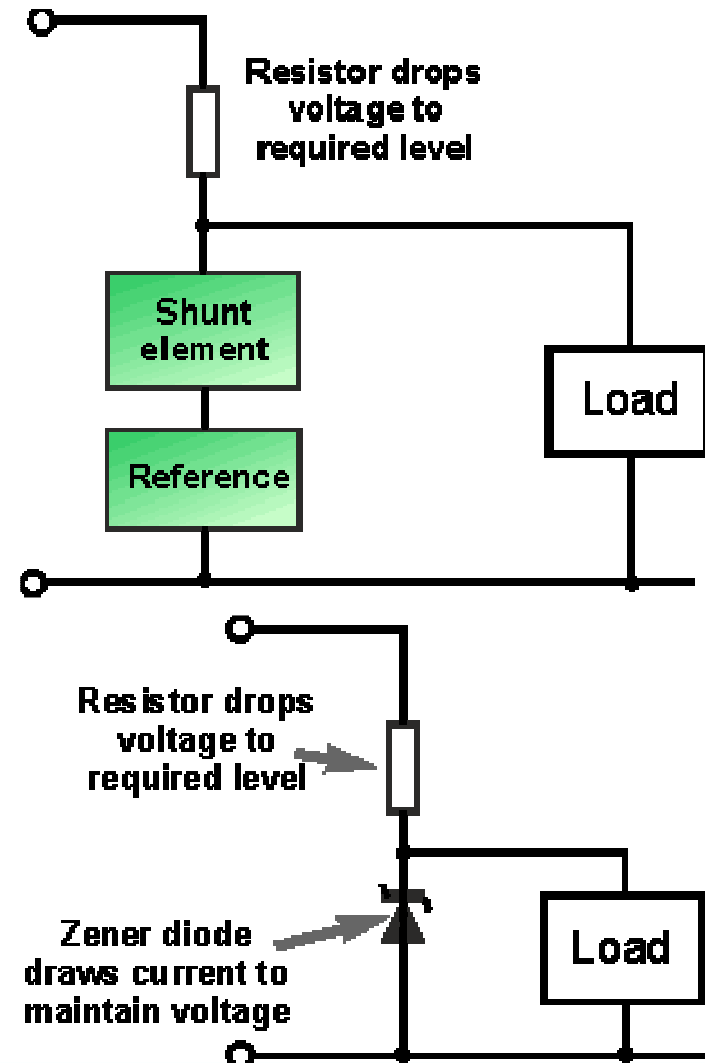
## Shunt Topology


- Maximum current is drawn from the source regardless of load
- Hence, inefficient
- Simplest Shunt Linear Voltage Regulator



# Switch-mode Regulator

- Buck or Boost
- Here is a Boost-mode Regulator



$$V_{out} > V_{in}$$

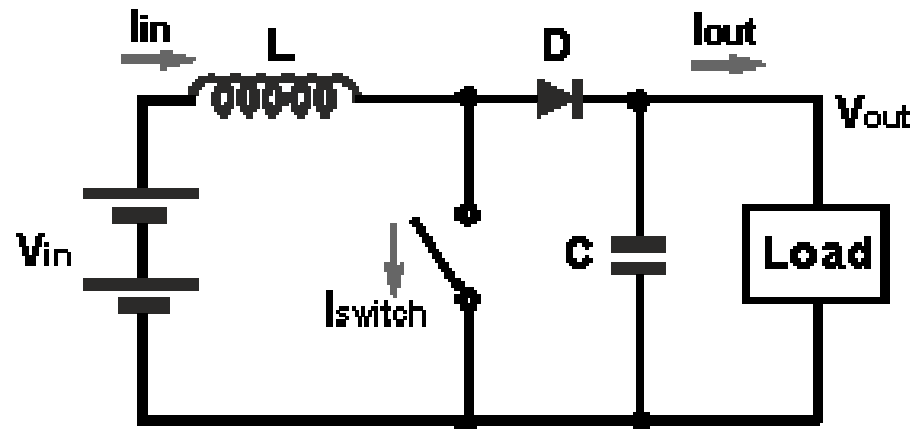

- Efficiencies of up to 90% are common

# The Bipolar Junction Transistor (BJT)

- Nonlinear device with three terminals:

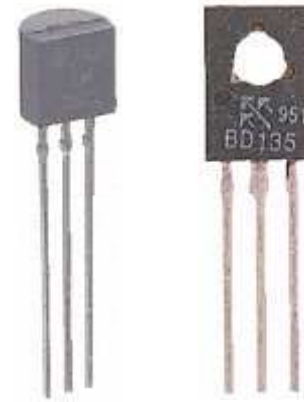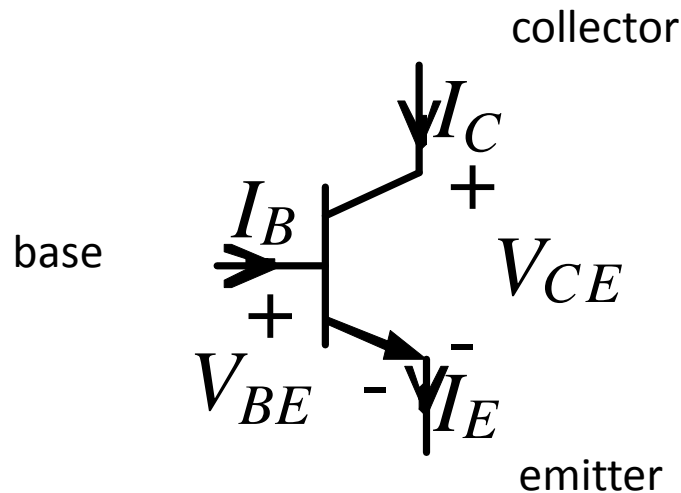


- Has several operating modes
  - $V_{BE} > 0.7V$ ,  $V_{CE} > 0.3V \Rightarrow$  forward active mode

source: <http://australia.rs-online.com>
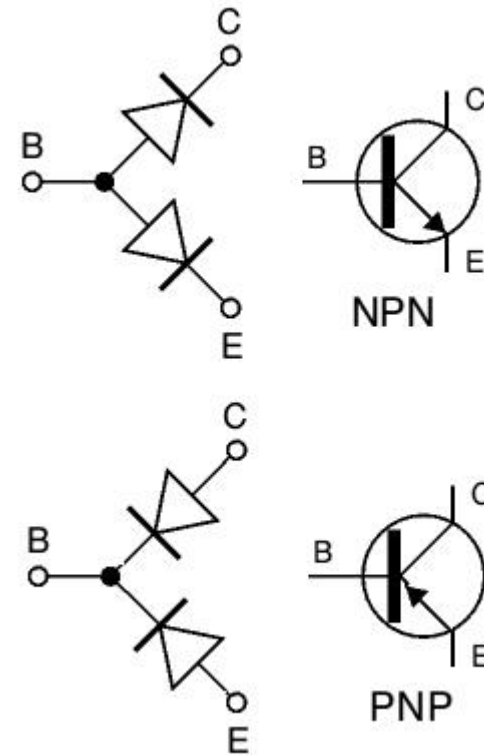
# Transistor as Two Diodes

- Two types – NPN and PNP
- Effectively a diode as C-B and B-E (two back to back PN junctions)
- PNP transistor has the N and P regions reversed
- Work the same way, but all polarities are the opposite for a PNP (versus an NPN)



source: [http://www.mobileelectronics.com.au/forums/index.php?/topic/58571-blown-jay-car-amp-help/page\\_\\_st\\_\\_15](http://www.mobileelectronics.com.au/forums/index.php?/topic/58571-blown-jay-car-amp-help/page__st__15)

# Transistor – Forward Active Mode

Most circuits aim to bias the transistor so it is in forward-active mode -> straight-forward to analyse

- $V_C > V_E$ , and BE junction forward-biased (CE junction reverse-biased)
- When conducting,  $V_B - V_E \approx 0.6\text{-}0.8\text{V}$  (forward-bias voltage)
- If the above is true, the current  $I_C$  will be proportional to the  $I_B$  current...

# Transistor Current Gain

- In forward active mode

$$I_C = \beta I_B$$

- $\beta$  (or  $H_{FE}$  or  $h_{FE}$ ) is the current gain
  - Typically large, e.g. 50 to 200
- A small input current ( $I_B$ ) can be used to control a large output current ( $I_C$  or  $I_E$ )

- Also

$$I_E = I_B + I_C = (\beta + 1)I_B = \frac{(\beta + 1)}{\beta} I_C$$


- Most current is going from collector  $\rightarrow$  emitter

# Transistor – Limitations

## Practical limitations of forward-active mode

- A transistor has maximum values of  $I_C$ ,  $I_E$ , and  $V_{CE}$  that it can handle
- The power dissipation is limited ( $I_C \cdot V_{CE}$ )
- The properties depend heavily on temperature
- The current gain,  $\beta$ , varies substantially within models -> don't build circuits that depend on this parameter
- Always limit the base current (since is a forward-biased diode BE)


# Transistor Switch

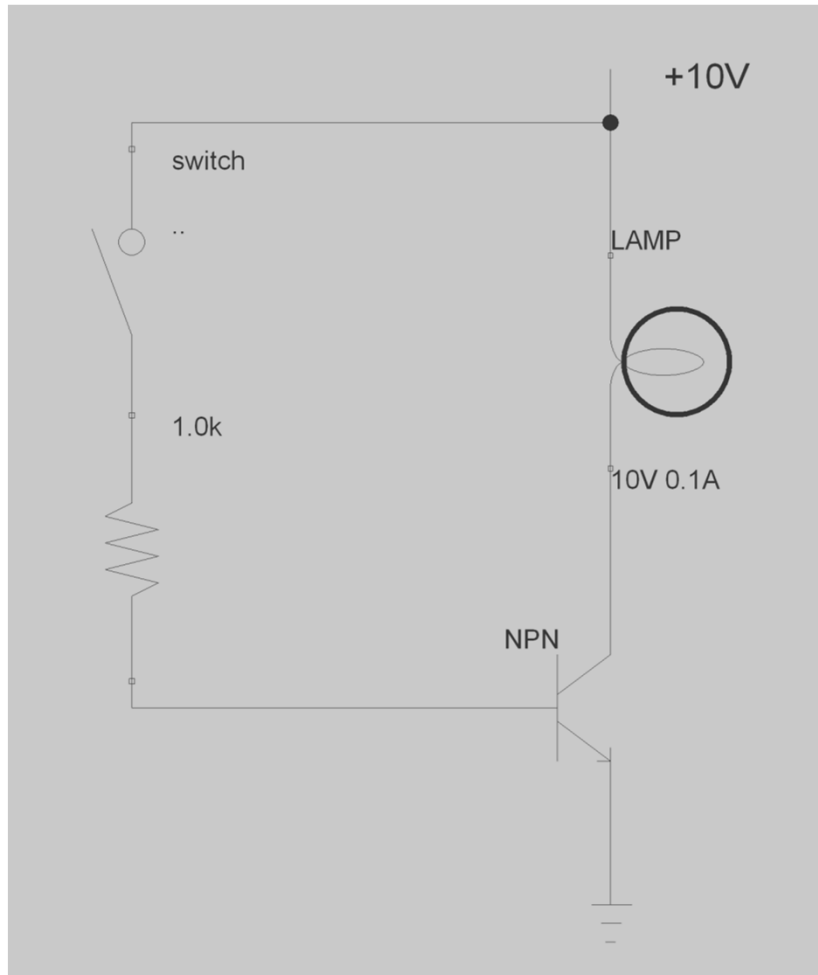

- When switch is open,  $I_B = 0$ , so  $I_{CE} = 0 \rightarrow$  lamp is off
- When switch is closed, how do we analyse this circuit?
- Assume the transistor is in forward-active mode
  - BE junction is conducting




# Transistor Switch

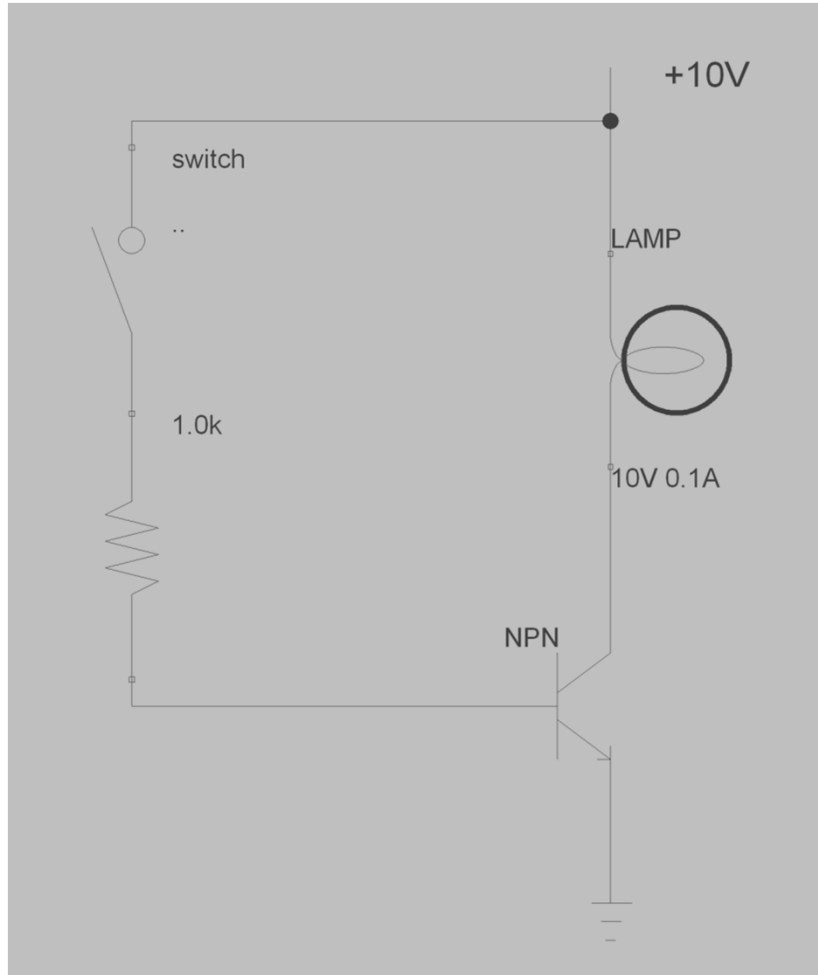

- $V_{BE} = 0.6V$
- $I_B = 9.4mA$
- If say,  $\beta = 100$ , then  $I_C = 940mA$ !
- But then  $V_C < 0 \rightarrow$  so transistor is not operating in the forward-active region
- Transistor here saturates

# Transistor Saturation

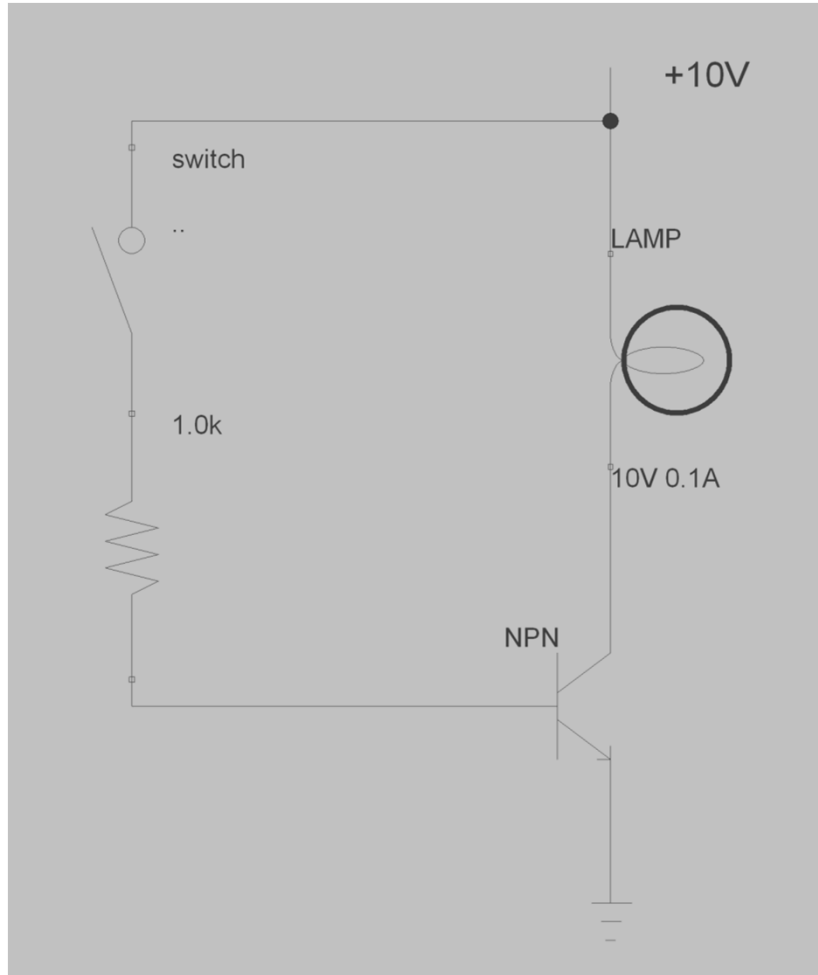


- Here,  $V_{CE}$  is forced as close to zero as it can go
  - Typical saturation voltages 0.05-0.2V
- Approx. 10V across the lamp, so  $I_C = 100\text{mA}$
- Note here – a small current (9.4mA) controls a large current (100mA)

# Voltage Sources

- Real voltage sources have internal resistance
- When a load is connected, the supplied voltage is really


$$V_O = \frac{R_L}{R_S + R_L} V_S$$

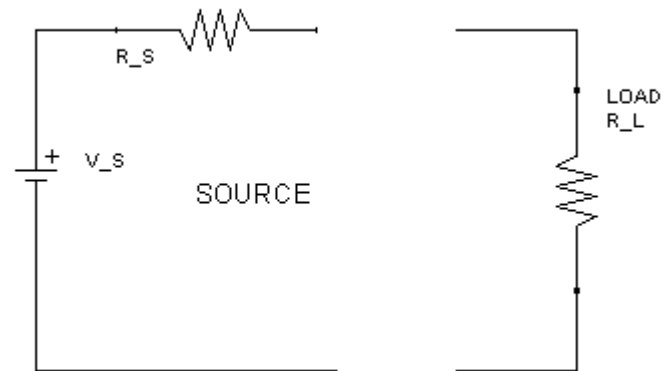

- The ideal is  $R_L \gg R_S$
- Important to realise this when you drive one circuit by another – may not always be possible!
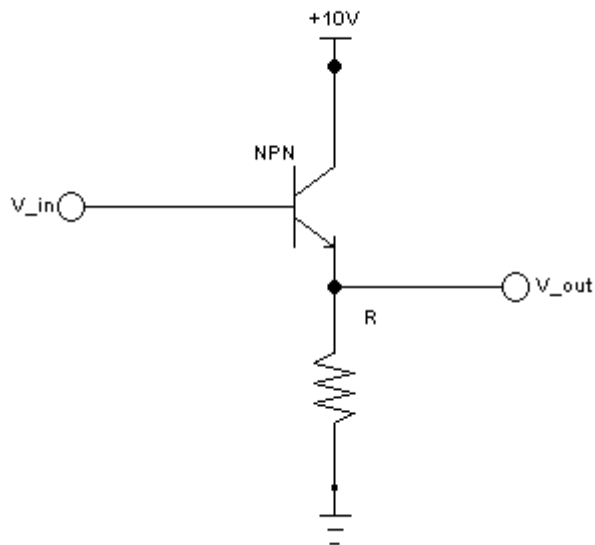
# Emitter Follower

- A simple transistor buffer circuit to connect between circuits to overcome the voltage-divider problem



- For input voltage
$$0.6V < V_{in} < 10V$$
- Transistor in the forward-active region
$$V_{out} = V_{in} - 0.6V$$
- So, what's the point?

# Emitter Follower

- The point is that the output impedance is significantly reduced  $\rightarrow R_L \gg R_S$ 
  - If you are going to connect something to the output, this external circuit sees a reduced source resistance
- Equivalently, the input impedance is significantly increased
  - If you think of  $V_{out}$  as the load, and you driving this with a circuit  $\rightarrow$  that external supply circuit sees a much larger  $R_L$

# Emitter Follower

- Input resistance is  $R_{in} = \frac{\Delta V_B}{\Delta I_B}$
- Output resistance is  $R_{out} = \frac{\Delta V_E}{\Delta I_E}$

Analysis:

- Since  $\Delta V_B = \Delta V_E$  and  $R = \frac{\Delta V_E}{\Delta I_E}$
- For the transistor in the forward-active region:

$$\Delta I_E = (\beta + 1)\Delta I_B$$


- Therefore,  $R_{in} = (\beta + 1)R_{out}$
- If we though the resistance seen by a load connected at  $V_{out}$ , when driven by a source of  $R_s$  at  $V_{in}$

$$R_{out} = \frac{1}{(\beta + 1)} R_s$$
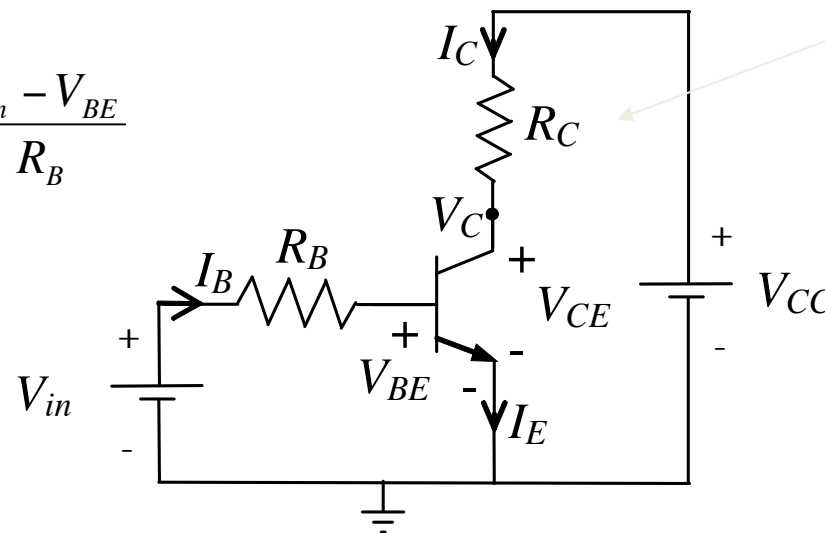
# Transistor circuit analysis

- Common-emitter configuration

$$I_C = \beta I_B = \beta \frac{V_{in} - V_{BE}}{R_B}$$



in many applications,  $R_C$  is the load

directly controlled by  $I_B$

constant

device constants

$$\text{output } V_C = V_{CC} - R_C I_C = V_{CC} - \beta R_C \frac{V_{in} - V_{BE}}{R_B}$$

constant, determined by design

# Transistors as switches

- Common-emitter configuration

$V_{in}$  large  $\rightarrow$  saturation

$\Rightarrow I_B$  large

$\Rightarrow I_C$  large

$\Rightarrow R_C I_C$  large

$\Rightarrow V_C$  small


$V_{in}$  small  $\rightarrow$  forward-active

$\Rightarrow I_B$  small

$\Rightarrow I_C$  small

$\Rightarrow R_C I_C$  small

$\Rightarrow V_C$  large

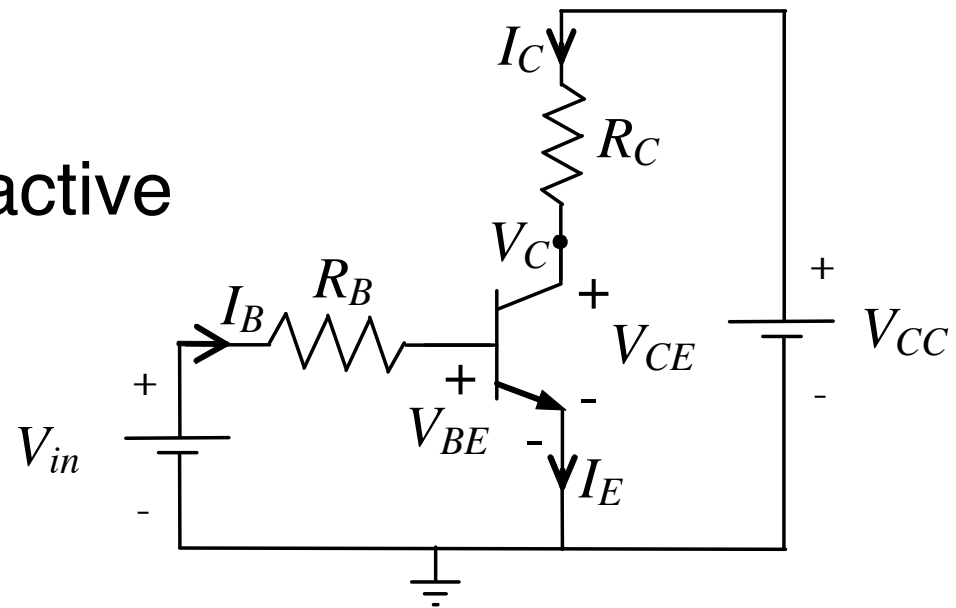




# Transistors as switches

- If  $V_{in}$  is large and  $R_C$  is chosen large enough, then the output  $V_C \approx 0$ 
  - “high” input  $\rightarrow$  “low” output
- If  $V_{in}$  is so small that  $V_{in} \leq V_{BE}$ , then the output  $V_C = V_{CC}$ 
  - “low” input  $\rightarrow$  “high” output
    - Note: if  $V_{in} < V_{BE}$ , actually the transistor is no longer in the forward active mode, and no current flows

# Transistor circuit analysis

- Common-collector configuration

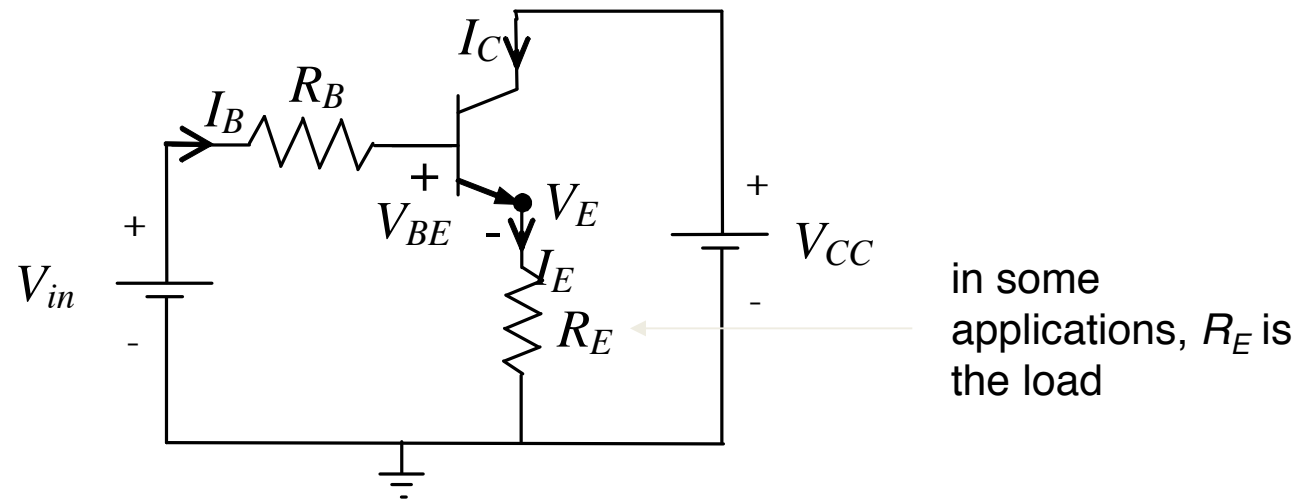

directly controlled by  $V_{in}$

constant design

device constant

$$V_E = V_{in} - V_{R_B} - V_{BE}$$

$$I_E = \frac{V_{in} - V_{BE}}{\frac{R_B}{\beta + 1} + R_E}$$

# Announcements

- Labs Open
  - Every Monday 2-6pm and Thursday 2-6pm
  - EE labs EEG14 and EE214
- Lab Exercises
  - Lab 1 this week – introduction
  - Labs 2, 3 & 4 available next week
  - Any one of them for 10%
  - Attend as convenient
- Lab Equipment
  - Breadboard would be ideal